

# Circuit Verification

CS386 Assignment: Group 12

Sahil Jindal  
110020043

Abhishek Gupta  
110040067

Rohan Gyani  
110040001

Mridul Ravi Jain  
110040083

# Assignment Specifications

- A circuit is defined by its input, output, gates and connectivity.
- There is circuit specific knowledge and circuit independent knowledge.
- Circuit independent knowledge is properties of gates (AND, OR, NOT etc) and the meaning of connectivity. You should read all this knowledge into the PROLOG memory.
- However, keep the circuit independent knowledge memory resident.
- The final goal is to verify the input and output in each row of the truth table


# Rules Defined

- `type(X, a).`
  - `a`: 'AND', 'OR', 'NOT', 'XOR'
  - Represents type of gate `X`
- `no_of_inputs(X, val).`
  - `val` : 1, 2, ....
  - Gate `X` has `val` inputs
- `count_1s(X , num_inputs, val, acc).`
  - Counts number of 1s as input to gate `X`
  - `num_inputs`: input index to gate `X`
  - `acc`: accumulator variable(initialised to zero)
  - `val`: final result is stored in this variable
- `signal(xn,a).`
  - Signal at  $x_n$  is a ( $x_n$  is input to circuit)

# Rules Defined

- `in(n,X, val).`
  - $n^{\text{th}}$  input to gate 'X' is 'val'
- `in(n,X).`
  - $n^{\text{th}}$  input to gate 'X'
- `connected(x1, x2).`
  - Used to specify connections in the circuit
  - Eg: `connected(x1,in(1,a1))`
    - x1 is connected to 1<sup>st</sup> input of gate a1
- `out(X,Val).`
  - Output of gate 'X' is stored in 'Val'
- `out(X).`
  - Output of gate 'X'

# 5-input Palindrome Circuit

 

$$\text{Output} = \overline{(x_0 \oplus x_4)} \cdot \overline{(x_1 \oplus x_3)}$$

# 5-input Weighted Majority Circuit

